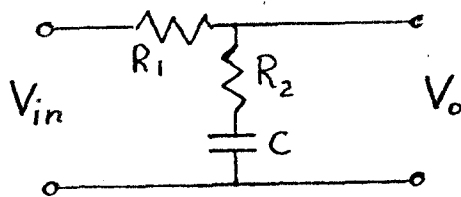


5. a. If $H(s) = V_o(s)/V_{in}(s)$ where $V_o(s)$ is the output voltage and $V_{in}(s)$ is the input voltage, $V_{in}(s) = Ae^{st}$ and $s = \sigma + j\omega$, find the $H(s)$ for the circuit shown below ($j = \sqrt{-1}$).





- b) Find the poles and zeros of $H(s)$.
- c) Make rough sketches of the frequency response of $H(j\omega)$ in the form: (1) $\log |H(j\omega)|$ vs. $\log \omega$ and (2) phase $H(j\omega)$ vs. $\log \omega$. Label any constant values and asymptotic slopes.
- d) It is possible for a closely related circuit to act as an ideal integrator. What $H(s)$ would be expected in that case?

$$a) H(s) = \frac{(R_2 + \frac{1}{sC})}{(R_1 + (R_2 + \frac{1}{sC}))} = \frac{1 + R_2 s}{1 + (R_1 + R_2)Cs}$$

$$b) \text{ zero: } s = -\frac{1}{R_2 C}$$
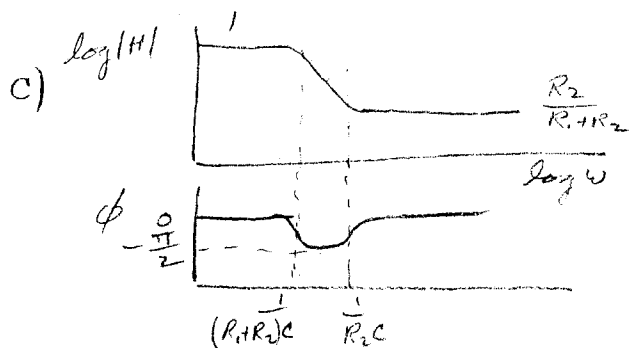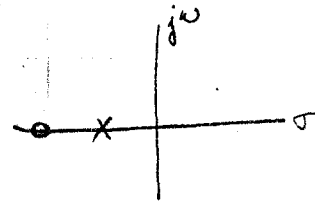
$$\text{pole: } s = -\frac{1}{(R_1 + R_2)C}$$



$$d) \int e^{st} = \frac{1}{s} e^{st}$$

$$\text{so } H(s) = \text{const} \cdot \frac{1}{s}$$